

# EECS 16A CSM Presentation


Bryan Ngo

2020-08-24

# The Voltage Divider

EECS 16A  
CSM  
Presentation

Bryan Ngo

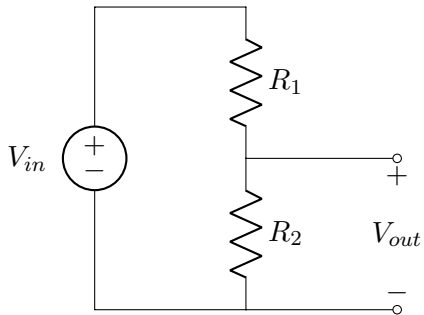


# Derivation

## Labeling

EECS 16A  
CSM  
Presentation

Bryan Ngo

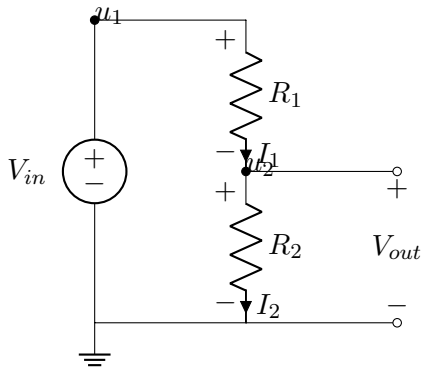

# Derivation (cont.)

## Node Voltage Analysis

EECS 16A  
CSM  
Presentation

Bryan Ngo

$$u_1 = V_{in} \quad (1)$$

$$u_2 = V_{out} \quad (2)$$

$$\frac{u_2}{R_2} - \frac{u_1 - u_2}{R_1} = 0 \quad (3)$$

$$\Rightarrow u_1 \left( -\frac{1}{R_1} \right) + u_2 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = 0 \quad (4)$$

$$V_{out} \left( \frac{R_1 + R_2}{R_1 R_2} \right) = V_{in} \left( \frac{1}{R_1} \right) \quad (5)$$

$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in} \quad (6)$$

# Demo

EECS 16A  
CSM  
Presentation

Bryan Ngo

`http://tinyurl.com/y2rqf523`