

EECS 16B CSM

Bryan Ngo

Computer Science Mentors

2021-02-24 & 2021-03-03

Overview

EECS 16B
CSM

Bryan Ngo

Filters

Bode Plots

1 Filters

2 Bode Plots

Logistics

EECS 16B
CSM

Bryan Ngo

Filters

Bode Plots

- internet whoopsie last week
- Pertinent facts

EECS 16B
CSM

Bryan Ngo

Filters

Bode Plots

Filters

Why?

EECS 16B
CSM

Bryan Ngo

Filters

Bode Plots

- allows us to isolate desired frequency ranges
- color organ: basically just a spectrogram
- Afrotechmods video

Types

EECS 16B
CSM

Bryan Ngo

Filters

Bode Plots

- low-pass: let in low ω
- high-pass: let in high ω
- band-pass: let in range of ω
- band-stop: block out range of ω

Transfer Functions

EECS 16B
CSM

Bryan Ngo

Filters

Bode Plots

$$H(j\omega) = \frac{V_{out}}{V_{in}} = \frac{(j\omega)^{N_z} \alpha_0 + (j\omega)\alpha_1 + \cdots + (j\omega)^n \alpha_n}{(j\omega)^{N_p} \beta_0 + (j\omega)\beta_1 + \cdots + (j\omega)^m \beta_m} \quad (1)$$

$$= K \frac{(j\omega)^{N_z} \left(1 + j\frac{\omega}{\omega_{z1}}\right) \left(1 + j\frac{\omega}{\omega_{z2}}\right) \cdots \left(1 + j\frac{\omega}{\omega_{zn}}\right)}{(j\omega)^{N_p} \left(1 + j\frac{\omega}{\omega_{p1}}\right) \left(1 + j\frac{\omega}{\omega_{p2}}\right) \cdots \left(1 + j\frac{\omega}{\omega_{pn}}\right)} \quad (2)$$

- N_z : number of zeroes
- N_p : number of poles
- ω_{zn} : n -th zero
- ω_{pn} : n -th pole

EECS 16B
CSM

Bryan Ngo

Filters

Bode Plots

Bode Plots



Definition

EECS 16B
CSM

Bryan Ngo

Filters

Bode Plots

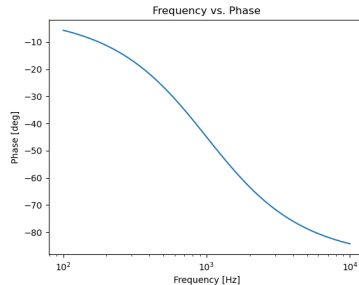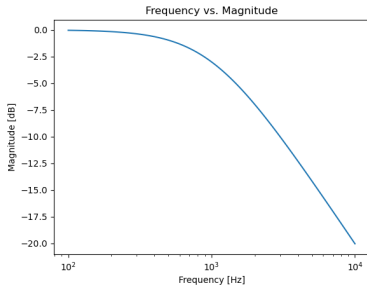

- comes in pairs: magnitude & phase
- above: low-pass filter

Features

EECS 16B
CSM

Bryan Ngo

Filters

Bode Plots

- magnitude

- x -axis: log frequency (Hz)
- y -axis: $|H(j\omega)|$ (dB or intensity)
- **cutoff frequency:** $|H(j\omega)| = \frac{1}{\sqrt{2}} = -3 \text{ dB}$

- phase

- x -axis: log frequency (Hz)
- y -axis: phase offset ($^\circ$ or rad)

Why?

EECS 16B
CSM

Bryan Ngo

Filters

Bode Plots

- allows us to characterize a filter very fast
- quick visual tool

Resonance

EECS 16B
CSM

Bryan Ngo

Filters

Bode Plots

- whenever you see an inductor & a capacitor
- energy is oscillating back and forth
- when voltage is at resonant frequency $\frac{1}{\sqrt{LC}}$, inductor and capacitor act as short