

# EECS 16B CSM

Bryan Ngo

UC Berkeley

2022-03-01

# Announcements

EECS 16B  
CSM

Bryan Ngo

Phasors

Filters

Bode Plots

- Pertinent facts
- Review session next Tuesday

EECS 16B  
CSM

Bryan Ngo

Phasors

Filters

Bode Plots

# Phasors

# Phasors

EECS 16B  
CSM

Bryan Ngo

Phasors

Filters

Bode Plots

- Encodes information about any sinusoid: voltage, current, etc.
- If frequency is constant, then uniquely identifies

$$x(t) = A \cos(\omega t + \phi) = \frac{A}{2} \left( e^{j(\omega t + \phi)} + e^{-j(\omega t + \phi)} \right) \quad (1)$$

$$= \frac{A}{2} \left( e^{j\omega t} e^{j\phi} + \overline{e^{j\omega t} e^{j\phi}} \right) \quad (2)$$

$$\iff \tilde{X} = \frac{A}{2} e^{j\phi} \quad (3)$$

# Properties

EECS 16B  
CSM

Bryan Ngo

Phasors

Filters

Bode Plots

Given  $x_1(t) = \tilde{X}_1 e^{j\omega t} + \overline{\tilde{X}_1 e^{j\omega t}}$ ,  $x_2(t) = \tilde{X}_2 e^{j\omega t} + \overline{\tilde{X}_2 e^{j\omega t}}$  with phasors  $\tilde{X}_{1,2}$ ,

- Uniqueness:  $x_1(t) = x_2(t) \implies \tilde{X}_1 = \tilde{X}_2$
- Linearity:  $a_1 x_1(t) + a_2 x_2(t) \implies a_1 \tilde{X}_1 + a_2 \tilde{X}_2$  for  $a_{1,2} \in \mathbb{R}$
- Differentiation:  $x(t) \iff \tilde{X} \implies \frac{d}{dt} x(t) = \frac{d}{dt} \left( \tilde{X} e^{j\omega t} + \overline{\tilde{X} e^{j\omega t}} \right) = j\omega \left( \tilde{X} e^{j\omega t} + \overline{\tilde{X} e^{j\omega t}} \right) \iff j\omega \tilde{X}$

# Circuits & Phasors

## KVL


EECS 16B  
CSM

Bryan Ngo

Phasors

Filters

Bode Plots

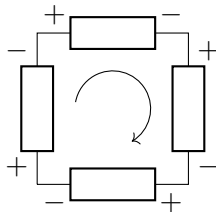

$$\sum_i \tilde{V}_i = 0 \quad (4)$$

# Circuits & Phasors (cont.)

## KCL


EECS 16B  
CSM

Bryan Ngo

Phasors

Filters

Bode Plots

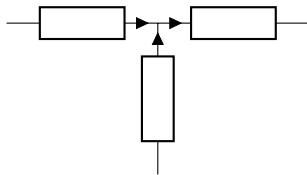

$$\sum \tilde{I}_{out} = \sum \tilde{I}_{in} \quad (5)$$

# Circuits & Phasors (cont.)

## Ohm's Law


EECS 16B  
CSM

Bryan Ngo

Phasors

Filters

Bode Plots

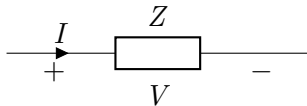

$$\tilde{V} = \tilde{I} \underbrace{Z}_{\text{impedance}}$$

(6)



# Passive Elements & Phasors


EECS 16B  
CSM

Bryan Ngo

Phasors

Filters


Bode Plots

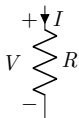

$$\tilde{V} = \tilde{I}R \quad (7)$$


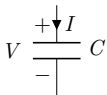
$$\tilde{V} = L \frac{d}{dt} \tilde{I} = j\omega L \tilde{I} \quad (8)$$



$$\tilde{I} = C \frac{d}{dt} \tilde{V} = j\omega C \tilde{V} \implies \tilde{V} = \frac{1}{j\omega C} \tilde{I} \quad (9)$$

EECS 16B  
CSM

Bryan Ngo

Phasors

**Filters**

Bode Plots

# Filters

# Why?

EECS 16B  
CSM

Bryan Ngo

Phasors

Filters

Bode Plots

- allows us to isolate desired frequency ranges
- color organ: basically just a spectrogram
- Afrotechmods video

# Types

EECS 16B  
CSM

Bryan Ngo

Phasors

Filters

Bode Plots

- low-pass: let in low  $\omega$
- high-pass: let in high  $\omega$
- band-pass: let in range of  $\omega$
- band-stop: block out range of  $\omega$

EECS 16B  
CSM

Bryan Ngo

Phasors

Filters

Bode Plots

# Bode Plots

# Definition



EECS 16B  
CSM

Bryan Ngo

Phasors

Filters

Bode Plots

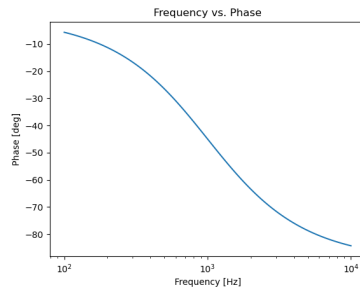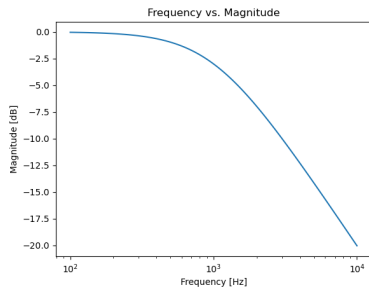

- comes in pairs: magnitude & phase
- above: low-pass filter

# Features

EECS 16B  
CSM

Bryan Ngo

Phasors

Filters

Bode Plots

- magnitude

- $x$ -axis: log frequency (Hz)
- $y$ -axis:  $|H(j\omega)|$  (dB or intensity)
- **cutoff frequency:**  $|H(j\omega)| = \frac{1}{\sqrt{2}} = -3 \text{ dB}$

- phase

- $x$ -axis: log frequency (Hz)
- $y$ -axis: phase offset ( $^\circ$  or rad)

# Why?

EECS 16B  
CSM

Bryan Ngo

Phasors

Filters

Bode Plots

- allows us to characterize a filter very fast
- quick visual tool



# Resonance

EECS 16B  
CSM

Bryan Ngo

Phasors

Filters

Bode Plots

- whenever you see an inductor & a capacitor
- energy is oscillating back and forth
- when voltage is at resonant frequency  $\frac{1}{\sqrt{LC}}$ , inductor and capacitor act as short