

EECS 16B CSM

Bryan Ngo

Computer Science Mentors

2020-09-21

- 1 Differential Equations
- 2 RC Circuits
- 3 Vector Differential Equations
- 4 Change of Basis
- 5 Inductors (Preview)

Logistics

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

- Quest?
- Focus for today?
- messenger chat
- all slides available at <https://github.com/bdngo/16b-csm>

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

Differential Equations

Differential Equations

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

Concept check!

Differential Equations

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

Concept check!

$$\frac{d}{dt}x(t) = f(x, t) \quad (1)$$

- Focusing on first-order ODEs
- Relates the derivative in other terms
- 3Blue1Brown video

Exponential Differential Equation

Homogeneous

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

$$\frac{d}{dt}x(t) = \lambda x(t) \implies x(t) = x_0 e^{\lambda t} \quad (2)$$

Exponential Differential Equation

Non-Homogeneous

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

$$\frac{d}{dt}x(t) = \alpha x(t) + \beta \quad (3)$$

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

RC Circuits

Undamped Response

EECS 16B
CSM

Bryan Ngo


Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

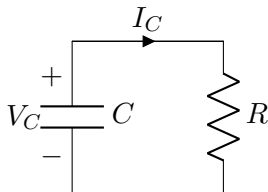

Undamped Response

EECS 16B
CSM

Bryan Ngo


Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

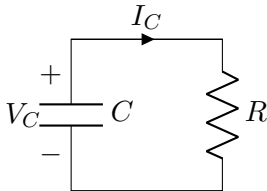

$$C \frac{d}{dt} V_C = -\frac{V_C}{R} \quad (4)$$

$$\frac{d}{dt} V_C = -\underbrace{\frac{1}{RC}}_{\lambda} V_C \quad (5)$$

$$\Rightarrow V_C(t) = V_0 e^{-\frac{1}{RC}t} = V_0 e^{-\frac{1}{\tau}t} \quad (6)$$

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

Vector Differential Equations

General Form

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

$$\frac{d}{dt}\mathbf{x}(t) = \mathbf{A}\mathbf{x}(t) + \mathbf{B}\mathbf{u}(t) \quad (7)$$

- if \mathbf{A} is diagonal, simply a bunch of exponential differential Equations
- if not, we can try to diagonalize

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

Change of Basis

Motivation

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

- conversion from one linear coordinate system to another
- Yet another 3Blue1Brown video

A Visualization

EECS 16B
CSM

Bryan Ngo


Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

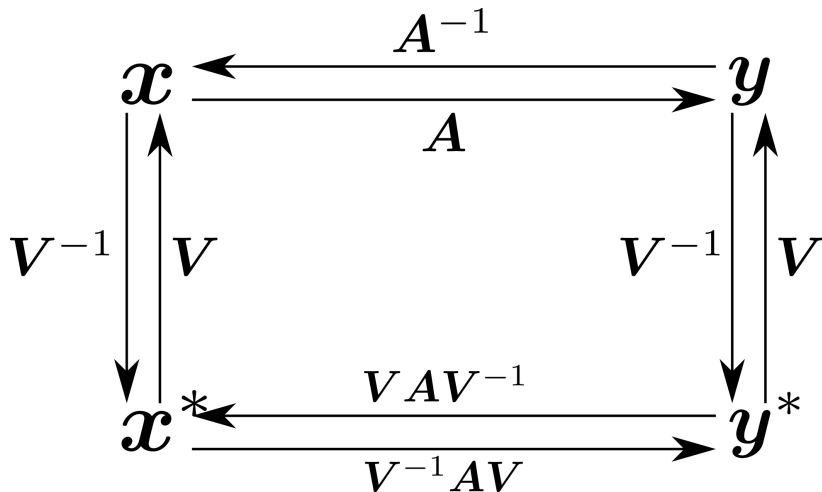

Diagonalization

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Vector
Differential
Equations

**Change of
Basis**

Inductors
(Preview)

- want the eigenvectors to be the basis for a vector space
- makes math way easier

Diagonalization

- want the eigenvectors to be the basis for a vector space
- makes math way easier

$$\mathbf{V} = \begin{bmatrix} \mathbf{v}_1 & \mathbf{v}_2 & \cdots & \mathbf{v}_n \end{bmatrix} \quad (8)$$

$$\mathbf{A}\mathbf{V} = \begin{bmatrix} \lambda_1 \mathbf{v}_1 & \lambda_2 \mathbf{v}_2 & \cdots & \lambda_n \mathbf{v}_n \end{bmatrix} \quad (9)$$

$$= \begin{bmatrix} \mathbf{v}_1 & \mathbf{v}_2 & \cdots & \mathbf{v}_n \end{bmatrix} \begin{bmatrix} \lambda_1 & 0 & \cdots & 0 \\ 0 & \lambda_2 & \cdots & 0 \\ \vdots & \vdots & \ddots & \vdots \\ 0 & 0 & \cdots & \lambda_n \end{bmatrix} \quad (10)$$

$$= \mathbf{V}\mathbf{\Lambda} \implies \mathbf{\Lambda} = \mathbf{V}^{-1}\mathbf{A}\mathbf{V} \quad (11)$$

Diagonalizing DEs

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

$$\frac{d}{dt}\mathbf{x}(t) = \mathbf{A}\mathbf{x}(t) + \mathbf{B}\mathbf{u}(t) \quad (12)$$

$$\frac{d}{dt}\mathbf{V}\mathbf{z}(t) = \mathbf{A}\mathbf{V}\mathbf{z}(t) + \mathbf{B}\mathbf{u}(t) \quad (13)$$

$$\Rightarrow \frac{d}{dt}\mathbf{z}(t) = \mathbf{V}^{-1}\mathbf{A}\mathbf{V}\mathbf{z}(t) + \mathbf{V}^{-1}\mathbf{B}\mathbf{u}(t) \quad (14)$$

$$= \mathbf{\Lambda}\mathbf{z}(t) + \mathbf{V}^{-1}\mathbf{B}\mathbf{u}(t) \quad (15)$$

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

Inductors (Preview)

Basic Properties

EECS 16B
CSM

Bryan Ngo


Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

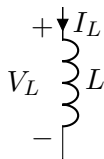

$$V_L = L \frac{d}{dt} I_L \quad (16)$$

- like a capacitor but for magnetic fields
- resists instantaneous change in current

Basic Properties

EECS 16B
CSM

Bryan Ngo


Differential
Equations

RC Circuits

Vector
Differential
Equations

Change of
Basis

Inductors
(Preview)

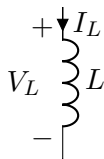

$$V_L = L \frac{d}{dt} I_L \quad (16)$$

- like a capacitor but for magnetic fields
- resists instantaneous change in current
- what happens when $\omega = 0$? $\omega = \infty$?