

EECS 16B CSM

Bryan Ngo

Computer Science Mentors

2020-09-14

Who am I?

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Transistors



- 2nd year majoring in EECS
- first time in CSM!
- took EECS 16B Spring 2020
- How I spent quarantine
 - lots of vidya (Hitman 2, Civ VI, Stellaris, etc.)
 - learned Haskell
 - building mechanical keyboard

Who are you?

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Transistors

- Name
- Pronouns
- Year/Major
- How you spent quarantine
- Most mundane/interesting fact about yourself

Logistics

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Transistors

- Join Piazza
- unexcused absences in first 3 weeks → **auto-dropped & NP**
- excused absences
 - email bryanngo@berkeley.edu & cc mentors@berkeley.edu with subject line [Request for Absence] <course>

Expectations

Me to You

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Transistors

- Be skeptical
- Constant feedback
- Become passionate about 16B

Expectations

You to Me

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Transistors

- Lecture:worksheet ratio?
- Get a webcam?
- Stop typing so loud?

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Transistors

Differential Equations

Differential Equations

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Transistors

Concept check!

Differential Equations

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Transistors

Concept check!

$$\frac{d}{dt}x(t) = f(x, t) \quad (1)$$

- Focusing on first-order ODEs
- Relates the derivative in other terms
- 3Blue1Brown video

Exponential Differential Equation

Homogeneous

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Transistors

$$\frac{d}{dt}x(t) = \lambda x(t) \implies x(t) = x_0 e^{\lambda t} \quad (2)$$

Exponential Differential Equation

Non-Homogeneous

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Transistors

$$\frac{d}{dt}x(t) = \alpha x(t) + \beta \quad (3)$$

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Transistors

RC Circuits

Undamped Response


EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Transistors

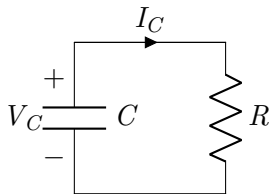

Undamped Response


EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Transistors

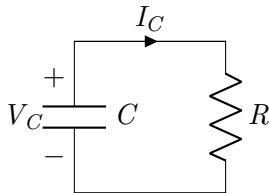

$$C \frac{d}{dt} V_C = -\frac{V_C}{R} \quad (4)$$

$$\frac{d}{dt} V_C = -\underbrace{\frac{1}{RC}}_{\lambda} V_C \quad (5)$$

$$\Rightarrow V_C(t) = V_0 e^{-\frac{1}{RC}t} = V_0 e^{-\frac{1}{\tau}t} \quad (6)$$

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Transistors

Transistors

NMOS & PMOS

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Transistors

