

EECS 16B CSM

Bryan Ngo

Computer Science Mentors

2022-02-08

1 Differential Equations

2 RC Circuits

3 Change of Basis

Who am I?

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Change of
Basis



- 3rd year majoring in EECS
- took EECS 16B Spring 2020
- Pertinent fact: watches too much AoT

Who are you?

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Change of
Basis

- Name
- Pronouns
- Year/Major
- Pertinent fact

Logistics

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Change of
Basis

- 2 unexcused absences during the semester
- excused absences: email bryanngo@berkeley.edu & cc.mentors@berkeley.edu with subject line [Request for Absence] <course>
- Slides available at <https://github.com/bdngo/16b-csm>



Expectations

Me to You

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Change of
Basis

- Be skeptical
- Constant feedback
- Become passionate about 16B

Expectations

You to Me

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Change of
Basis

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Change of
Basis

Differential Equations

Differential Equations

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Change of
Basis

Concept check!

Differential Equations

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Change of
Basis

Concept check!

$$\frac{d}{dt}x(t) = f(x, t) \quad (1)$$

- Focusing on first-order ODEs
- Relates the derivative in other terms
- 3Blue1Brown video

Exponential Differential Equation

Homogeneous

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Change of
Basis

$$\frac{d}{dt}x(t) = \lambda x(t) \implies x(t) = x_0 e^{\lambda t} \quad (2)$$

Exponential Differential Equation

Non-Homogeneous

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Change of
Basis

$$\frac{d}{dt}x(t) = \alpha x(t) + \beta \quad (3)$$

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Change of
Basis

RC Circuits

Undamped Impulse Response


EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Change of
Basis

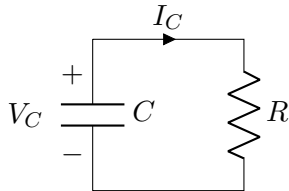

Undamped Impulse Response


EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Change of
Basis

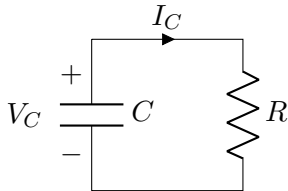

$$C \frac{d}{dt} V_C = -\frac{V_C}{R} \quad (4)$$

$$\frac{d}{dt} V_C = -\underbrace{\frac{1}{RC}}_{\lambda} V_C \quad (5)$$

$$\Rightarrow V_C(t) = V_0 e^{-\frac{1}{RC}t} = V_0 e^{-\frac{1}{\tau}t} \quad (6)$$

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Change of
Basis

Change of Basis

Motivation

EECS 16B
CSM



Bryan Ngo

Differential
Equations

RC Circuits

Change of
Basis

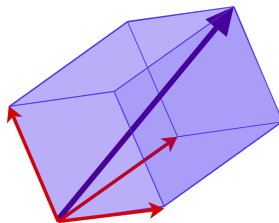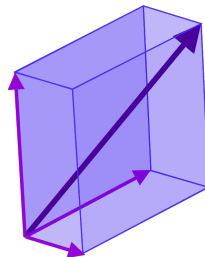- conversion from one linear coordinate system to another
- 3Blue1Brown video



A Visualization

EECS 16B
CSM

Bryan Ngo

Differential
Equations

RC Circuits

Change of
Basis

